

الاسم: عبد الرحمن محمد سالم

سكشن: 1

بیش نمبر: 38

Question 2

$$\Rightarrow T_{PLH} = R_{on2} C_L \left[\frac{2|V_{th2}|}{V_{DD} - |V_{th2}|} + \ln \left(3 - 4 \frac{|V_{th2}|}{V_{DD}} \right) \right]$$

$$\therefore T_{PLH} = 70 \text{ fs} = 70 \times 10^{-15}$$

$$\therefore 70 \times 10^{-15} = R_{on2} \times 1 \times 10^{-12} \left[\frac{2 \times 3.63214}{12 - 3.63214} + \ln \left(3 - \frac{4 \times 3.63214}{12} \right) \right]$$

$$\therefore R_{on2} = 48.28 \times 10^{-3} \quad \left\{ R_{on} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})} \right.$$

$$\therefore \frac{W}{L} = \frac{1}{48.28 \times 10^{-3} \times 5.22109 \times (5 - 12 - 3.63214)}$$

$$\therefore \left(\frac{W}{L} \right)_{PMOS} = 0.254 \rightarrow \text{for PMOS}$$

$$\Rightarrow T_{PHL} = R_{on1} C_L \left[\frac{2V_{th1}}{V_{DD} - V_{th1}} + \ln \left(3 - 4 \frac{V_{th1}}{V_{DD}} \right) \right]$$

$$\therefore T_{PHL} = 70 \text{ fs} = 70 \times 10^{-15}$$

$$70 \times 10^{-15} = R_{on1} \times 1 \times 10^{-12} \times \left[\frac{2 \times 1.72558}{12 - 1.72558} + \ln \left(3 - 4 \times \frac{1.72558}{12} \right) \right]$$

$$R_{on1} = 0.057 \quad \left\{ R_{on} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})} \right.$$

$$\therefore \frac{W}{L} = \frac{1}{0.240544 \times 0.057 \times (12 - 0 - 1.72558)} = 7.081$$

$$\therefore \left(\frac{W}{L} \right)_{NMOS} = 7.081$$

